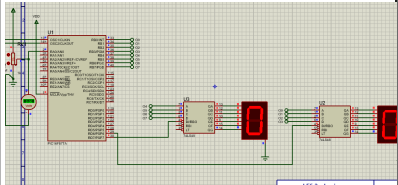
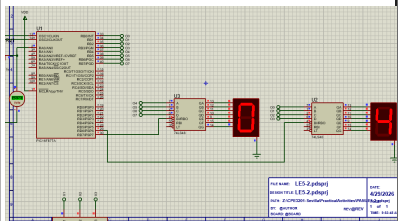
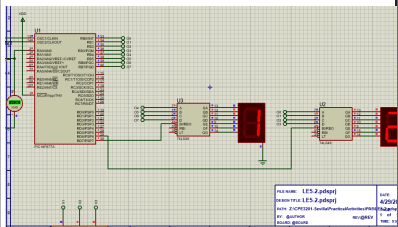
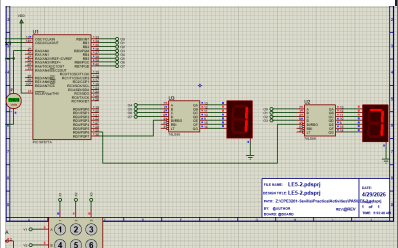
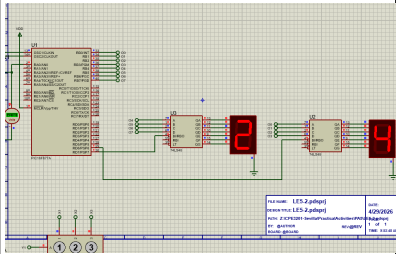
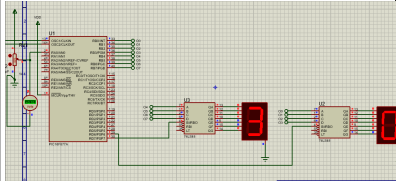
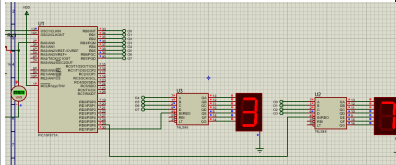
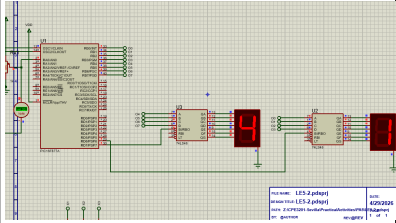
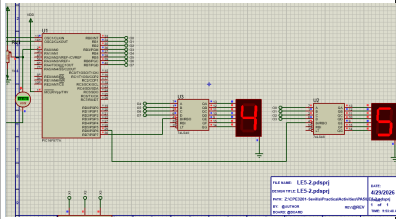
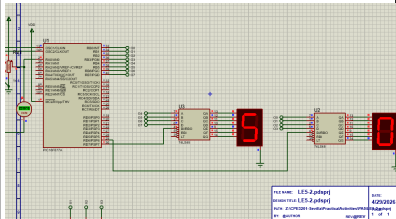


Sam ple	Input Voltage (Proteus Voltmeter)	Displayed Voltage (7-Segment Displays)	
1	0.00 V	0.0	
2	0.50 V	0.4	
3	1.25 V	1.2	
4	1.75 V	1.7	

5	2.50 V	2.4	
6	3.10 V	3.0	
7	3.75 V	3.7	
8	4.20 V	4.1	

9	4.60 V	4.5	 The circuit diagram shows a microcontroller-based system with a digital display showing 4.60 V. The display is connected to a microcontroller via a bus. The microcontroller is also connected to a power supply and a ground. The display is a 7-segment display with a red LED. The microcontroller is a small integrated circuit with multiple pins. The power supply is a 5V regulator. The ground is connected to the common ground of the display and the microcontroller.
10	5.00 V	5.0	 The circuit diagram shows a microcontroller-based system with a digital display showing 5.00 V. The display is connected to a microcontroller via a bus. The microcontroller is also connected to a power supply and a ground. The display is a 7-segment display with a red LED. The microcontroller is a small integrated circuit with multiple pins. The power supply is a 5V regulator. The ground is connected to the common ground of the display and the microcontroller.